


DSP Resources

- Specialized FPGA columns for complex arithmetic functionality
- DSP48 Tile: two DSP48 slices, interconnect
- Each DSP48 is a self-contained arithmetic-logical unit with add/sub/multiply/logic operations

DSP Resources

- DSP columns are, whenever possible, paired with Block RAM columns
- DSP48 tiles line up with RAMB36 (36Kb Block RAM)
- DSP48 slices line up with RAMB18
- Setup results in very fast routing from Block RAM to DSP slices

DSP Resources

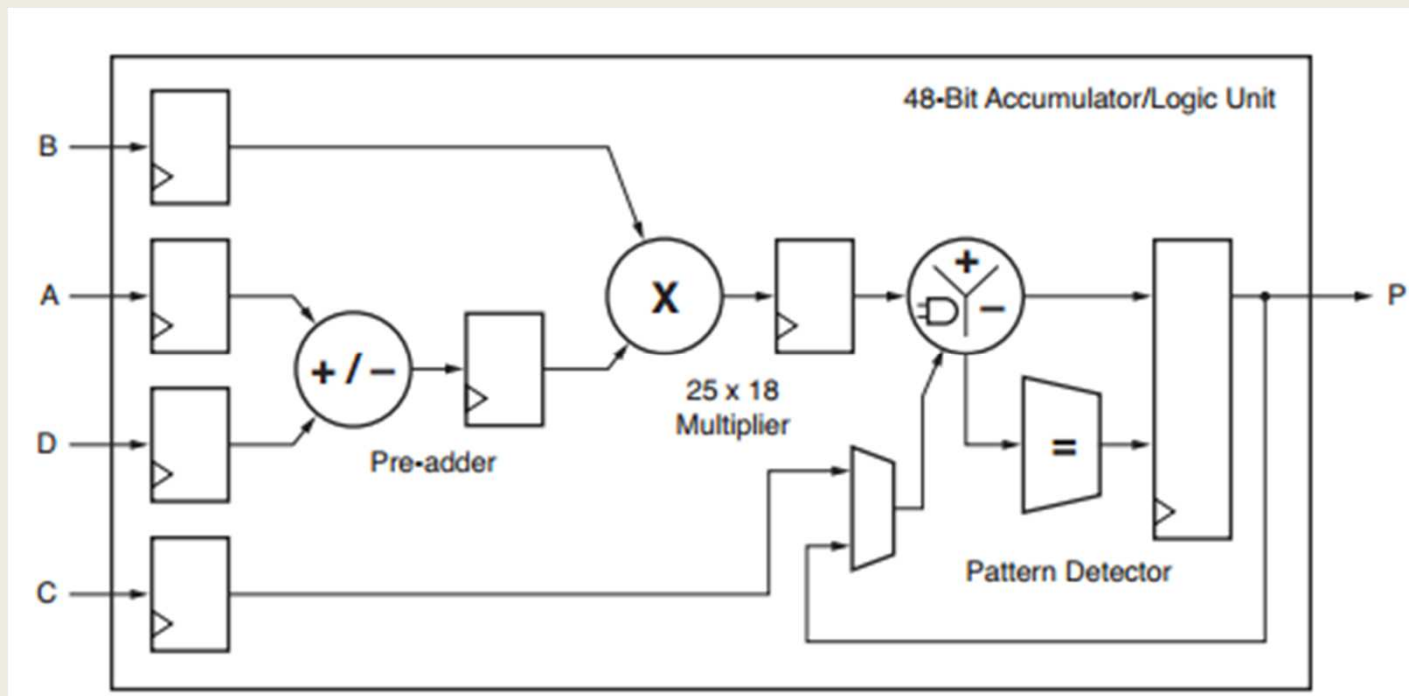


- Main features: 1 adder-subtractor, 1 multiplier, 1 add/sub/logic ALU, 1 comparator, several pipeline stages

Common DSP48 Applications

- Generic multiplication
- Generic Multiply-Accumulate: $y = \sum_i a(i)b(i)$
- FIR Filters: $y(n) = \sum_j^{N-1} c(j)x(n-j)$
 - symmetric coefficients: $c(j) = \pm c(N-1-j)$
- Barrel shifters
- Replacing fabric adder trees with fast adder cascades

DSP48 Slice

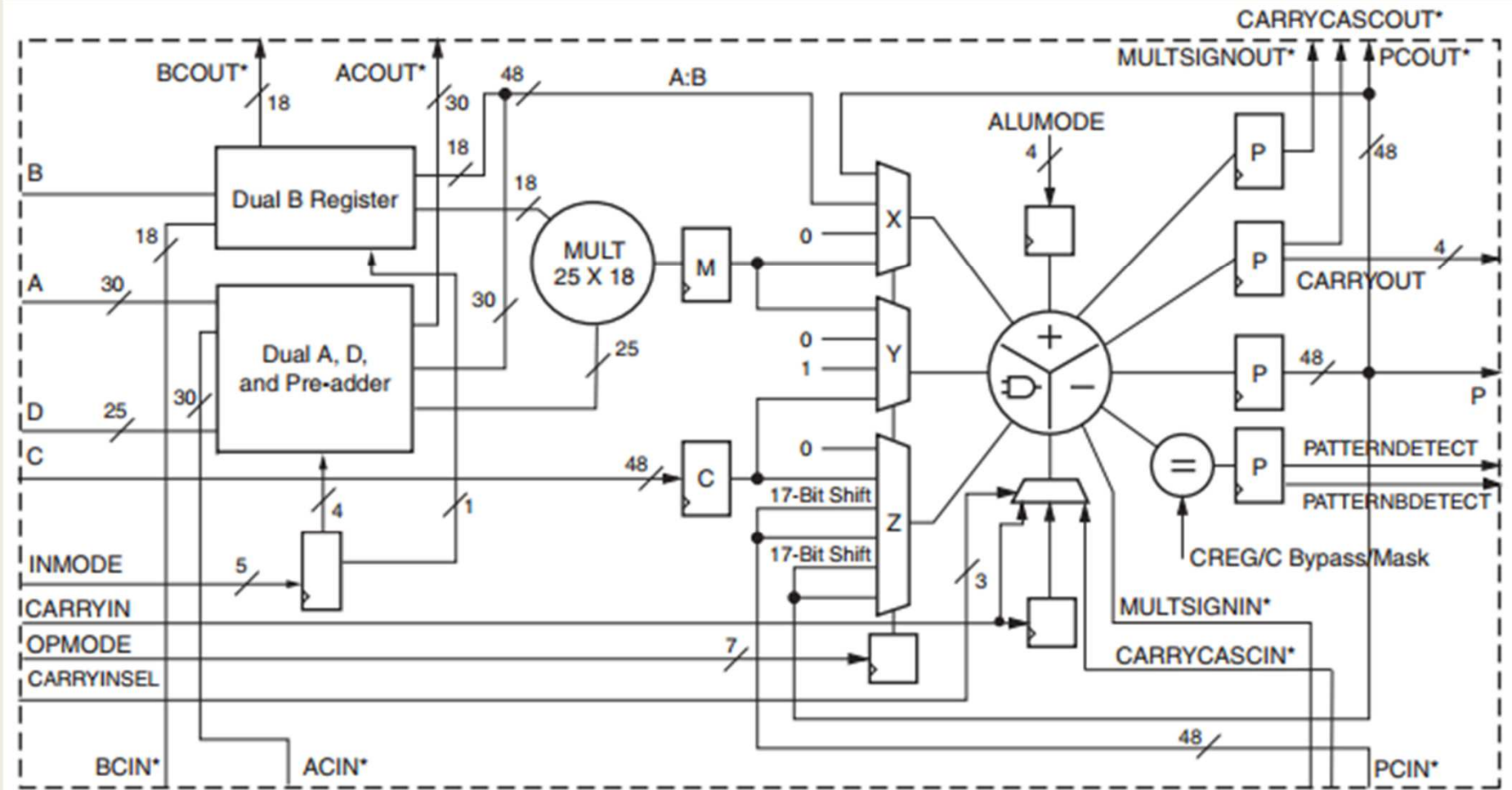


DSP48 Slice

- 4 main control signals:
 - INMODE (5b) controls pre-adders and input registers
 - OPMODE (7b) controls X, Y, Z multiplexers
 - CARRYINSEL (3b) controls source of carry for the final ALU
 - ALUMODE (4b) controls ALU function
- Each has positive clock-enable, synchronous positive reset (OPMODE and CARRYINSEL share control signals)


DSP48 Slice: Input Preadder Block

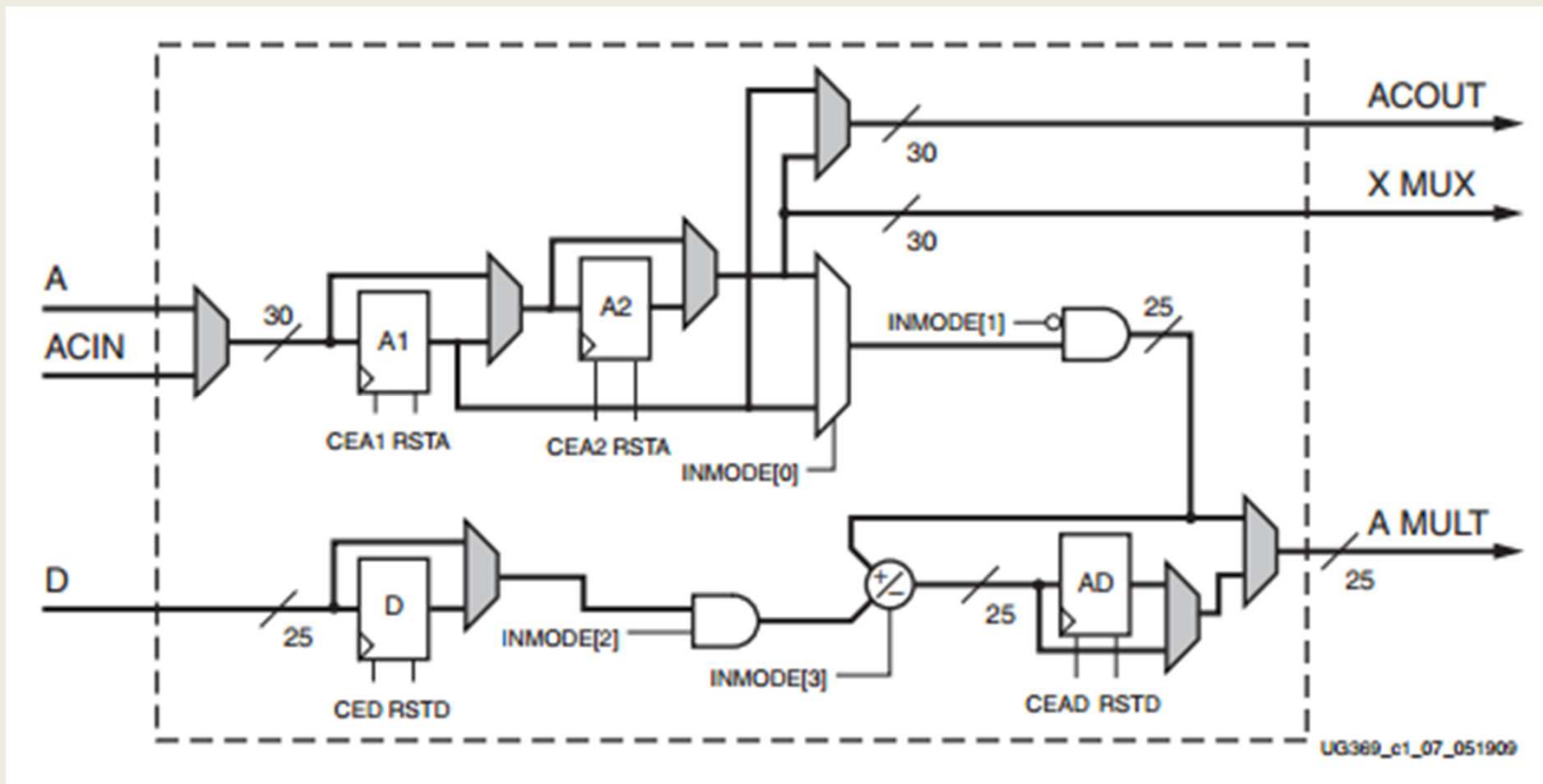- Preadder on A, D inputs
- Pipeline registers




DSP48 Slice: Input Pipeline Block

- Pipeline on on B input

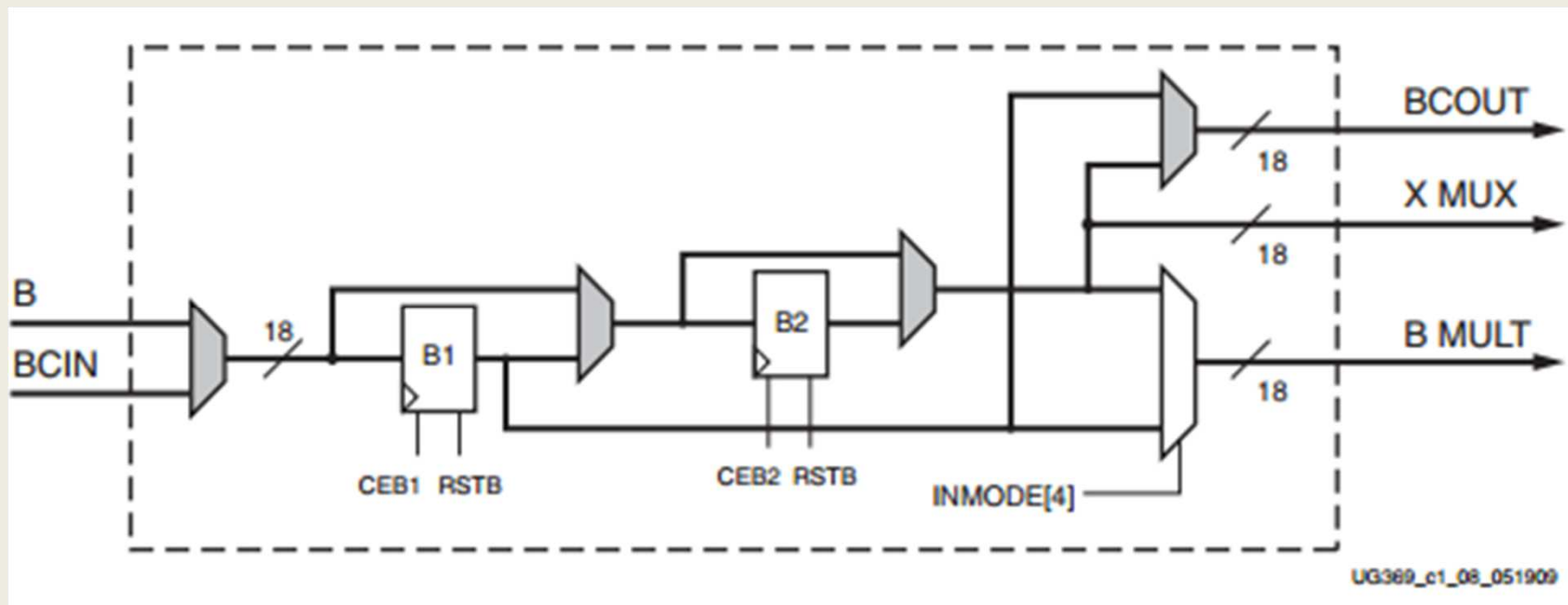

DSP48E1 Slice: Multiplexers

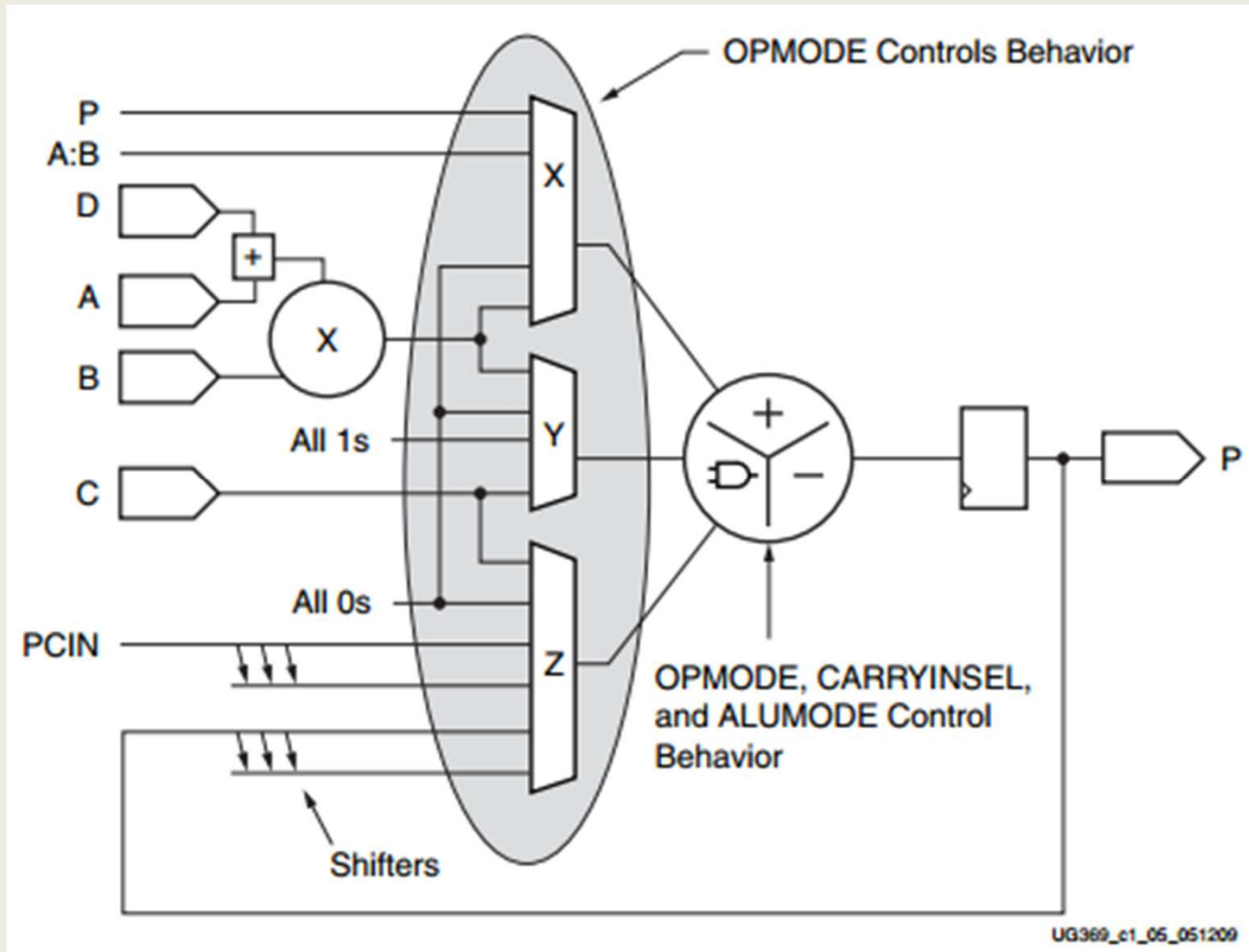

DSP48E1 Slice: ALU


- 2 Modes: 3-input and 2-input
- 3-Input mode (arithmetic):

ALUMODE	Function
4'd0	$X+Y+Z+CIN$
4'd1	$X+Y+CIN-Z-1$
4'd2	$-X-Y-Z-CIN-1$
4'd3	$Z-(X+Y+CIN)$

- 2-Input mode (logic): 16 logic functions between X and Z

DSP48E1 Slice: ALU

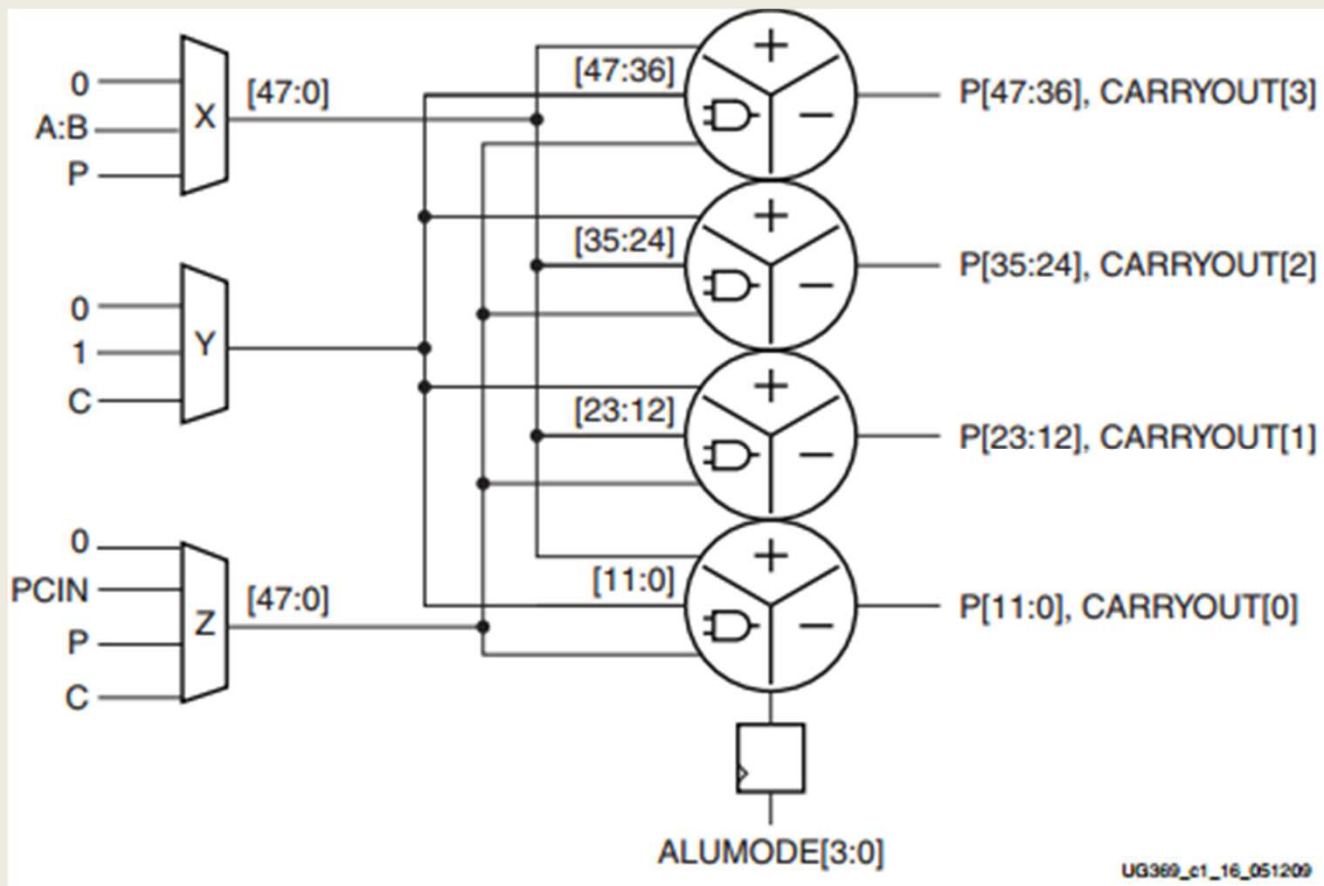- Arithmetic can be segmented into 2 or 4 SIMD



HDL Guide to Multipliers

- Described using multiplication operator (“*”)
 - Can be combinatorial or registered
- Implemented as fabric (LUTs) or DSP48 slices based on operand size
 - Per-device thresholds
 - Virtex-7: 6x6 bit multiplier in fabric, larger in DSP48
- DSP48 multiplication is natively signed
 - 18x25 bit signed multiplication
 - 17x24 unsigned multiplication (sign bit set to zero)

HDL Guide to Multipliers

- Pipeline registers can be absorbed into the DSP48 slice
 - Up to 2 output pipeline levels
 - Control signals: synchronous positive reset, positive enable

```
always @(posedge clock) begin
    if(reset) begin
        result_r1 <= 0;
        result_r2 <= 0;
    end else if(en) begin
        result_r1 <= op_a * op_b;
        result_r2 <= result_r1;
    end
end
```

HDL Guide to Multipliers

- Preadd-multipliers

```
always @(posedge clock)
```

```
  if(reset)
```

```
    if(en) begin
```

```
      preadd <= op_b + op_c;
```

```
      result_r1 <= op_a * preadd;
```

```
      result_r2 <= result_r1;
```

```
    end
```

- Adder, multiplier and all pipeline stages absorbed into a DSP48 slice
- Same result for pre-subtraction

HDL Guide to Multipliers

- Preaddsub-multipliers (?)

```
always @(posedge clock)
  if(reset) begin
    mult_in_preadd <= 0;
    result_r1 <= 0;
    result_r2 <= 0;
  end else if(en) begin
    if(paddsub)
      mult_in_preadd <= op_b - op_c;
    else
      mult_in_preadd <= op_b + op_c;
    result_r1 <= op_a * mult_in_preadd;
    result_r2 <= result_r1;
  end
```

HDL Guide to Multipliers


- Preaddsub-multipliers
 - B and C operands do not exceed 25 bits
 - Paddsub control signal selects subtraction when high (fabric inverter inserted if not)
 - Optionally, a clock-enabled register on paddsub input can be absorbed to improve timing
 - Because paddsub controls part of the INMODE register in the DSP48 slice, and INMODE is reset as a whole, reset is not available for paddsub only
 - Use of reset will result in fabric Flip-Flop for paddsub
 - Clock-enable can be dedicated

HDL Guide to MAC

- Multiply-accumulate block with pre-adder
 - Multiplication result can be accumulated into 48-bit result output
 - 32 samples accumulation at maximum multiplication operand size (32-stage FIR)
- Related function: preaddsub-multiply-postaddsub
 - multiplier output added or subtracted from 48-bit input
 - Switching operands results in fabric postaddsub
 - Postaddsub control signals same as preaddsub


HDL Guide to DSP48 Adder Cascades

 - Adder trees can only be implemented in fabric
 - Asymptotically optimal delay $O(\log N)$
 - Slow speed (f_{max})
 - Consumes Resources
 - Wastes Power
 - 8-input adder tree (48b): $\sim 4ns$ delay and 336 LUTs



HDL Guide to DSP48 Adder Cascades

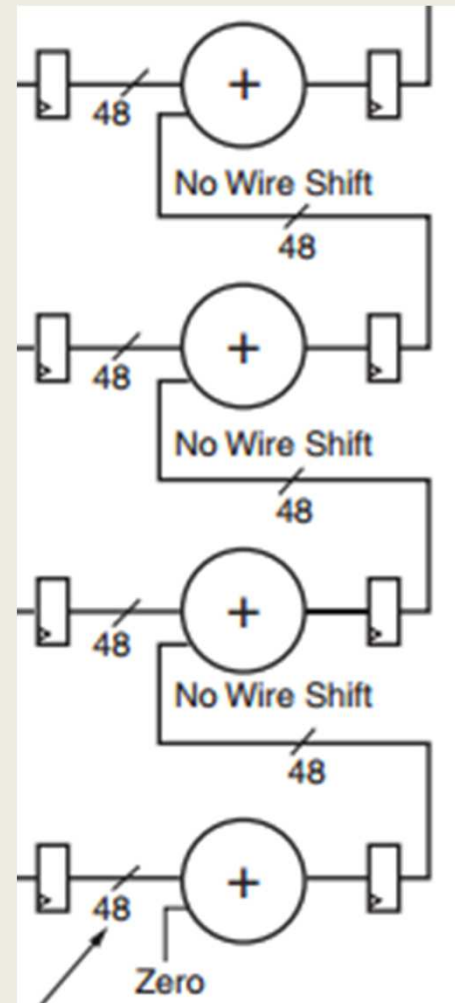- Adder cascades
 - Non-optimal delay $O(N)$
 - Fast speed (f_{max})
 - Requires only DSP48 resources
 - 8-input, 48b adder tree converts to 7-stage adder cascade @700MHz: ~10ns delay (7 DSP48 slices)




HDL Guide to DSP48 Barrel Shifters

- Traditional way to code barrel shifter:
`assign sh = (input << amount) | (input >> amount)`
- 16-bit input results in 48-LUT implementation
- Idea: use shift-by-multiply:
`assign mult = input * (1 << amount)`
`assign sh = mult[15:0] | mult[31:16]`
- Implemented using 1 DSP48 and 32 LUTs
- If amount is already decoded: 1 DSP48, 16 LUTs


HDL Guide to DSP48 Barrel Shifters

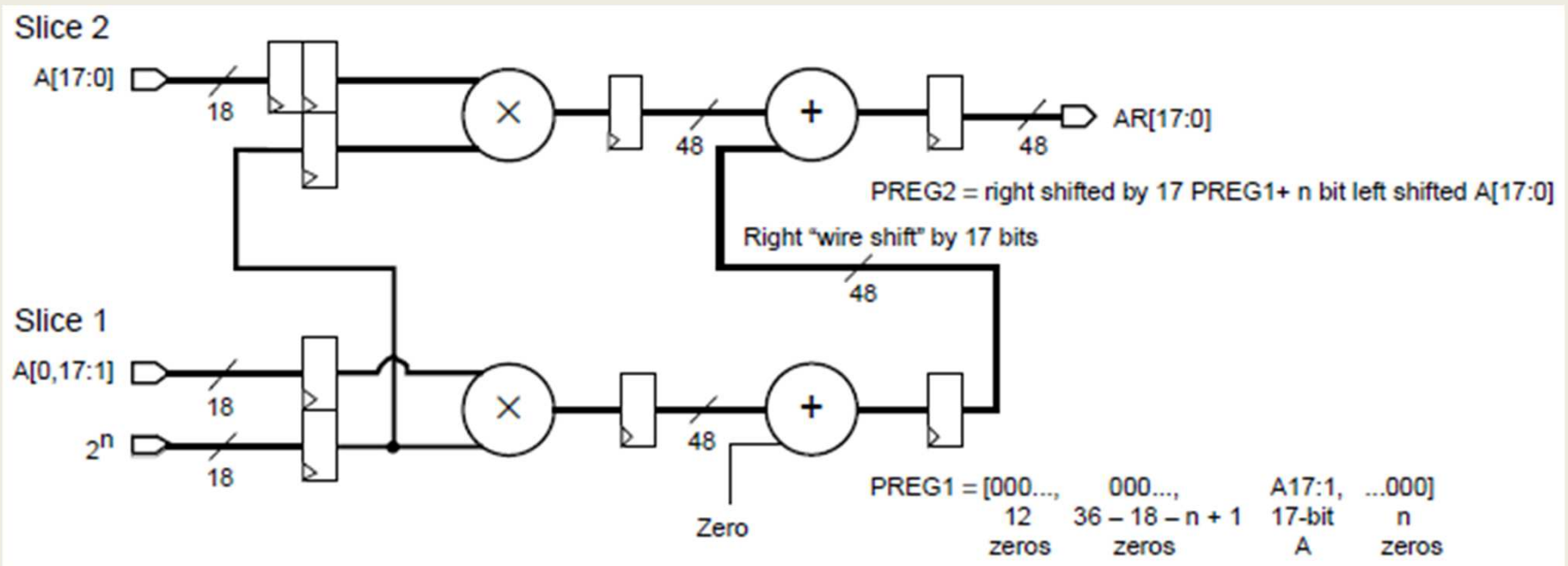- Eliminate LUTs by using DSP48 built-in wire shift and adders



HDL Guide to DSP48 Barrel Shifters

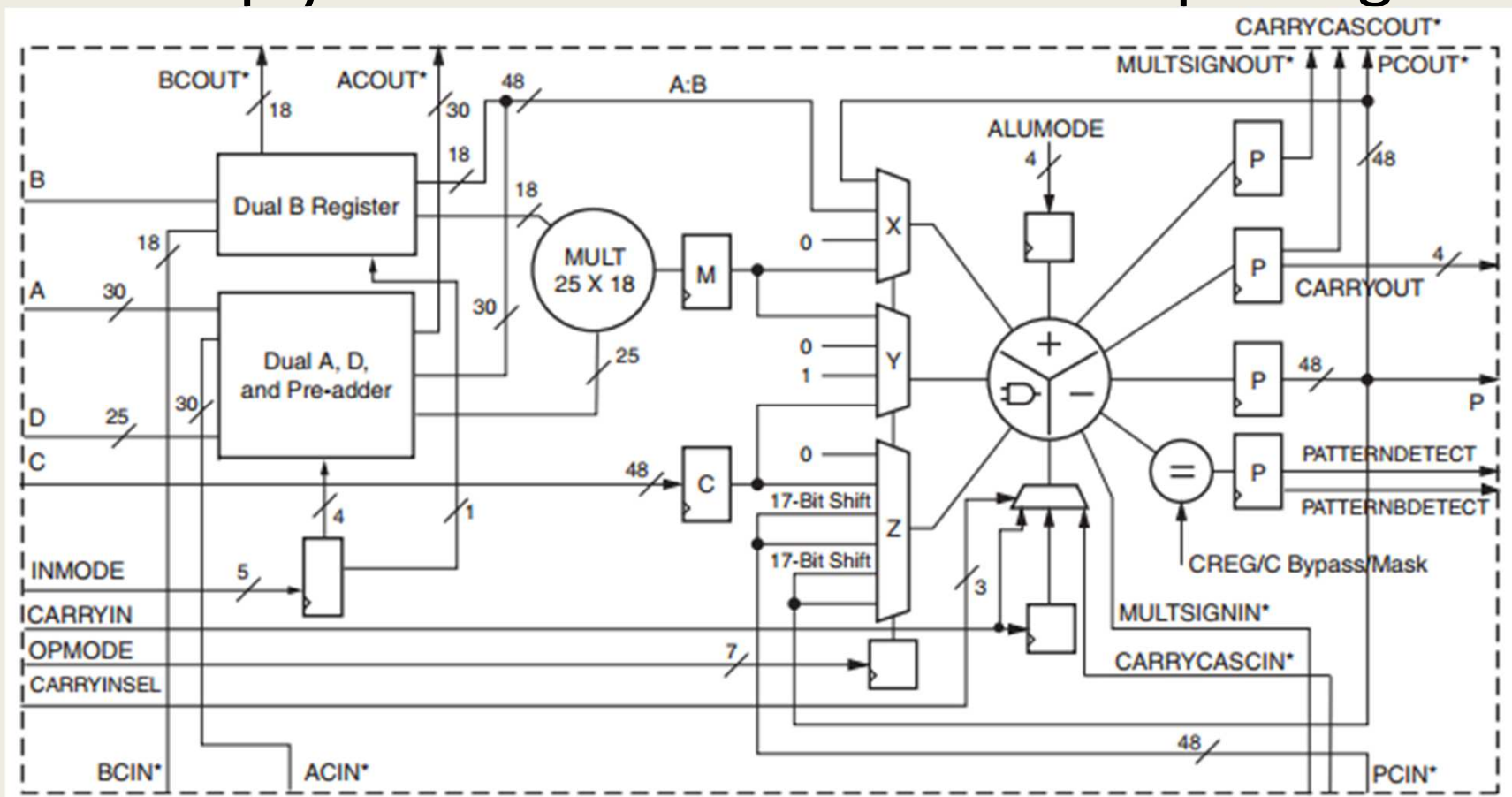- Implement in single DSP48 slice using multiply-accumulate and time multiplexing



Exercise: Complex Number Multiplier using DSP48 Slices

- $X = a + bj$
- $Y = c + dj$
- Compute $X*Y$ and report resource utilization, fmax

Further Reading

- [Virtex-4 FPGA XtremeDSP User Guide](#)
- [7-Series FPGA DSP Resources User Guide](#)
- [DSP: Designing for Optimal Results](#)