

# **Chapter 6**


**Frequency response of circuits.**

**Stability**

## **6.1. The frequency response of elementary functions**

## **6.1.1. The frequency bandwidth**


## 6.1.1. The frequency bandwidth

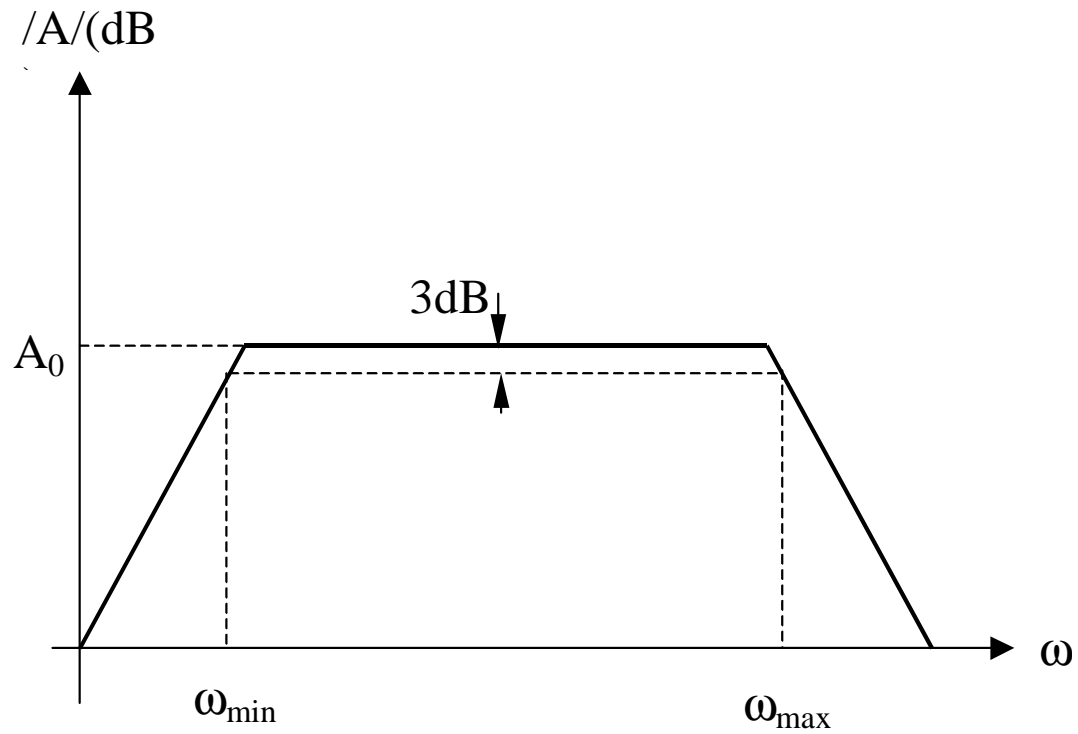

## **6.1.2. The frequency response of elementary functions**


## 6.1.2. The frequency response of elementary functions

### A constant

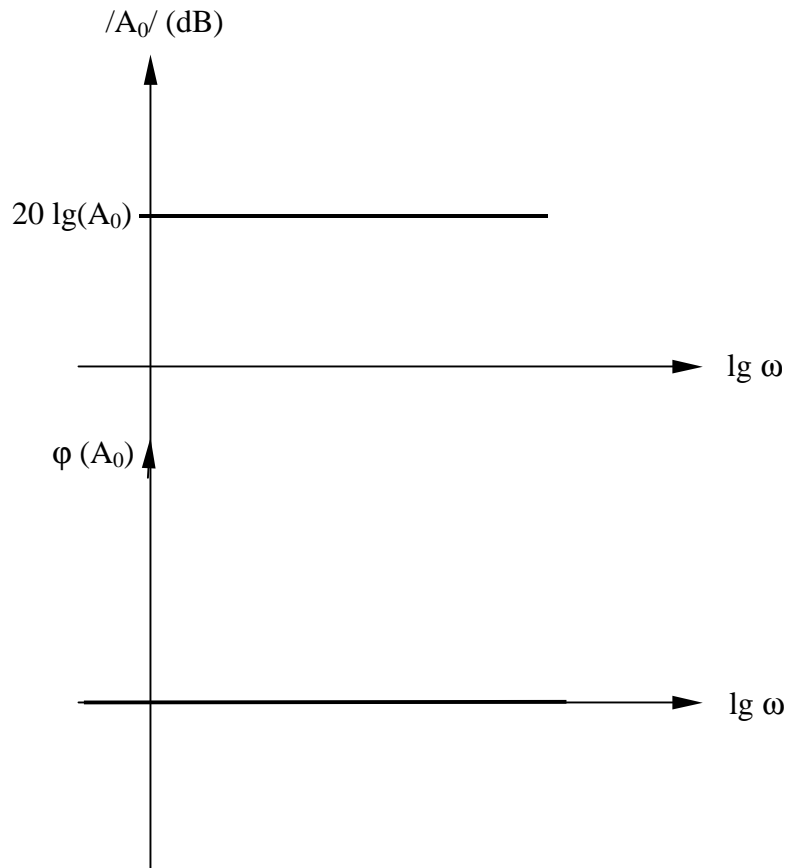

$$A_0 = ct.$$

# A simple zero

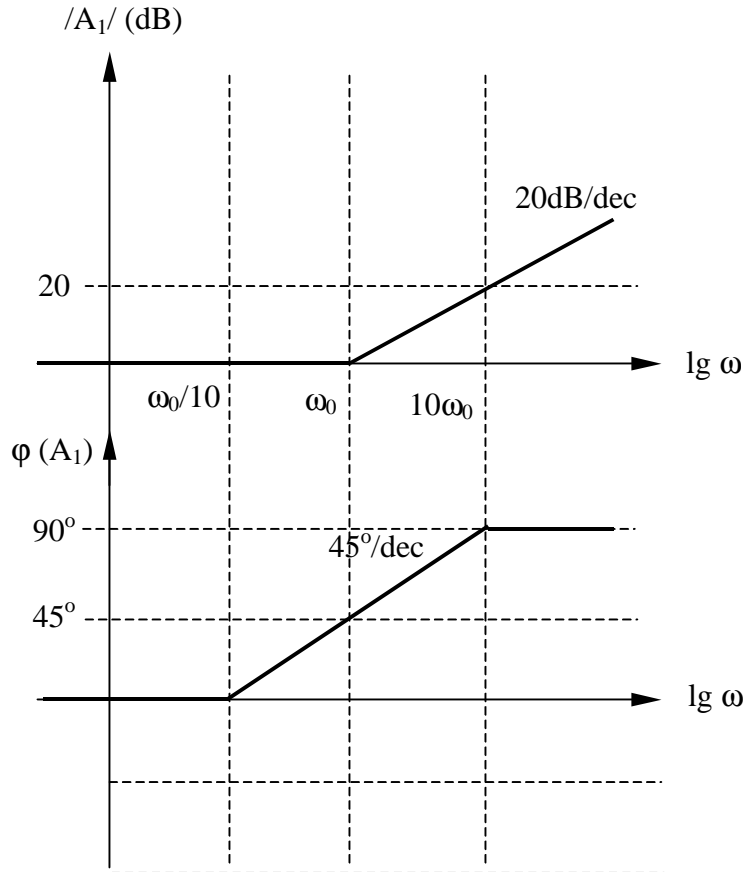

$$A_1 = 1 + j \frac{\omega}{\omega_0}$$


$$|A_1| = 20 \lg \left[ \sqrt{1 + \left( \frac{\omega}{\omega_0} \right)^2} \right]$$

$$\omega \ll \omega_0 \Rightarrow |A_1| \rightarrow 0$$

$$\omega \gg \omega_0 \Rightarrow |A_1| \rightarrow 20 \lg \left( \frac{\omega}{\omega_0} \right)$$

$$\varphi(A_1) = \arctg \left( \frac{\omega}{\omega_0} \right)$$

# A simple pole

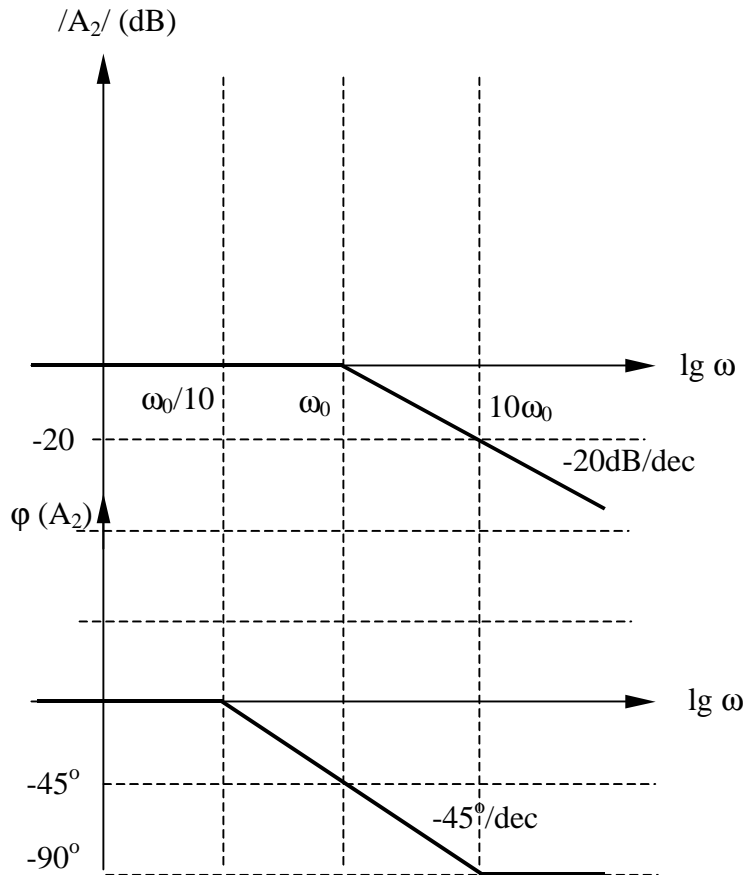

$$A_2 = \frac{1}{1 + j \frac{\omega}{\omega_0}}$$

$$|A_2| = -20 \lg \left[ \sqrt{1 + \left( \frac{\omega}{\omega_0} \right)^2} \right]$$


$$\omega \ll \omega_0 \Rightarrow |A_2| \rightarrow 0$$

$$\omega \gg \omega_0 \Rightarrow |A_2| \rightarrow -20 \lg \left( \frac{\omega}{\omega_0} \right)$$

$$\varphi(A_2) = -\arctg \left( \frac{\omega}{\omega_0} \right)$$



# A simple zero in origin

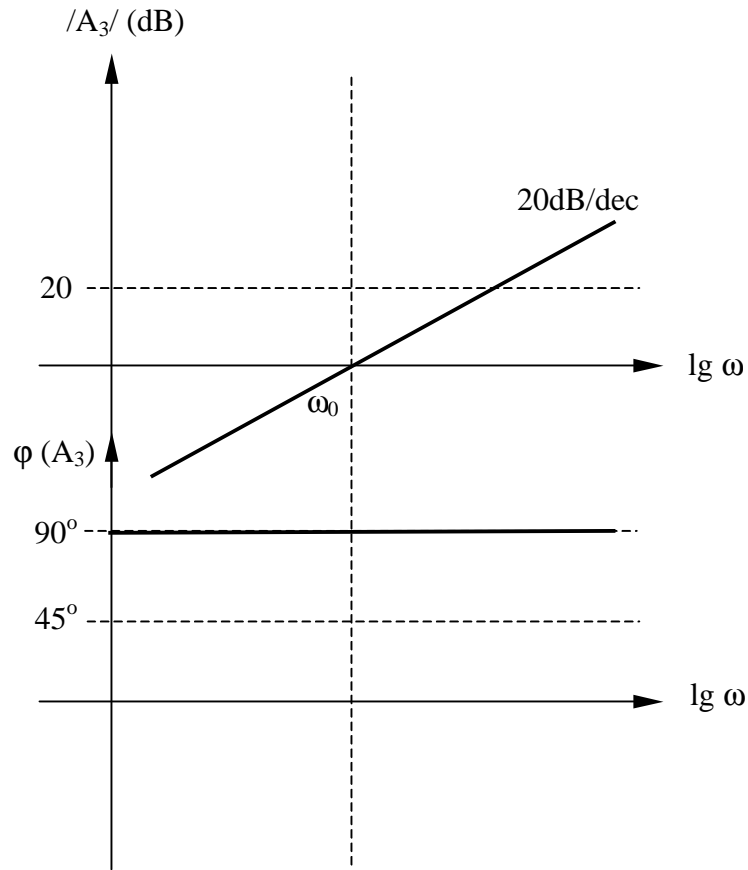


$$A_3 = j \frac{\omega}{\omega_0}$$

$$|A_3| = 20 \lg \left( \frac{\omega}{\omega_0} \right)$$

$$\varphi(A_3) = 90^\circ$$

# A simple pole in origin

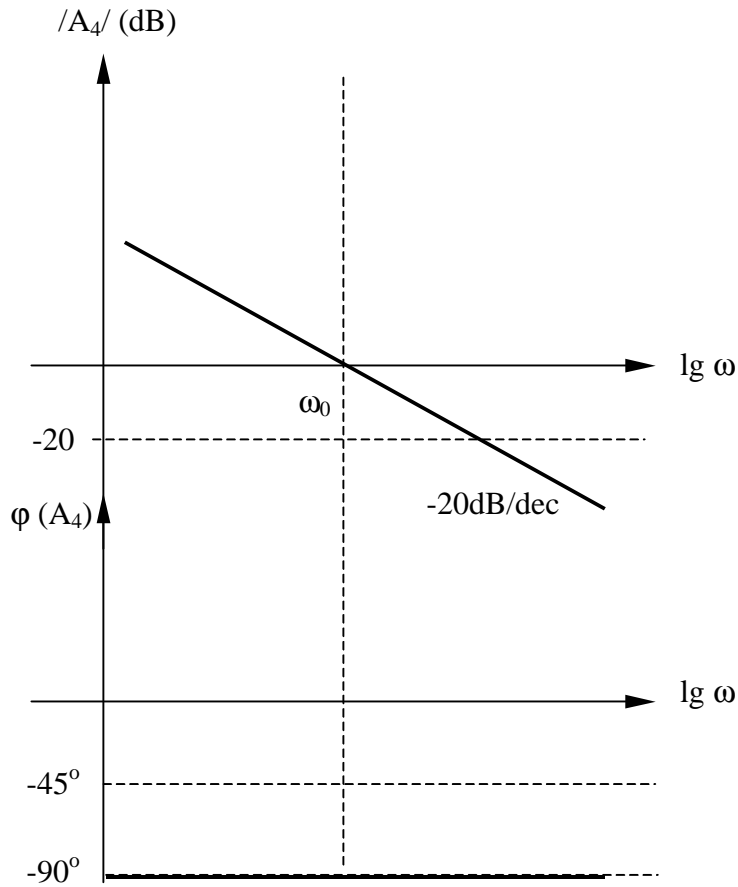


$$A_4 = \frac{1}{j \frac{\omega}{\omega_0}}$$

$$|A_4| = -20 \lg \left( \frac{\omega}{\omega_0} \right)$$

$$\varphi(A_4) = -90^\circ$$

# A multiple zero in origin

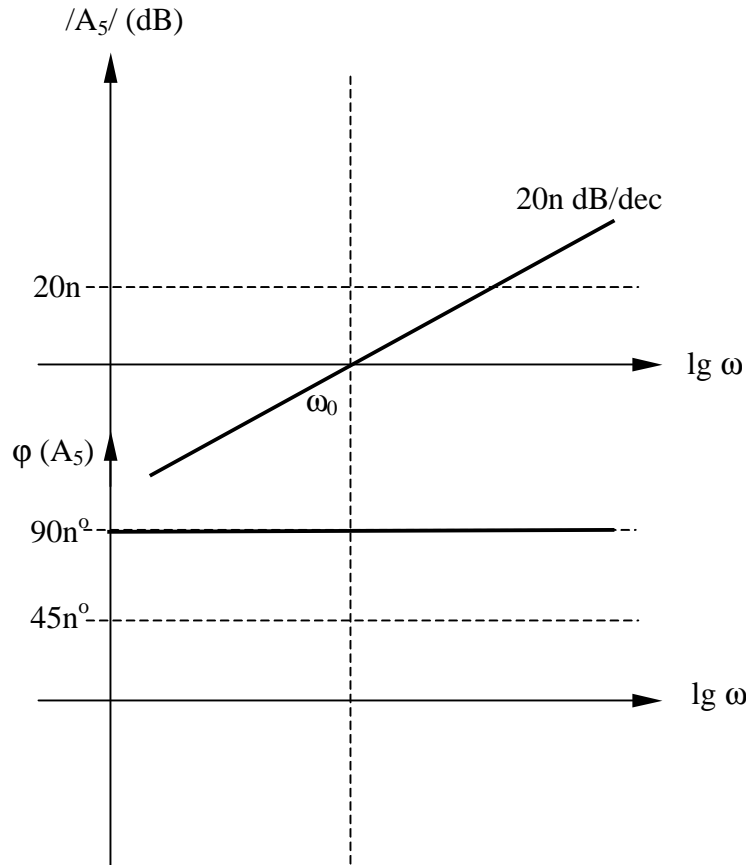


$$A_5 = \left( j \frac{\omega}{\omega_0} \right)^n$$

$$|A_5| = 20 \times n \lg \left( \frac{\omega}{\omega_0} \right)$$

$$\varphi(A_5) = n \times 90^\circ$$

# A multiple pole in origin

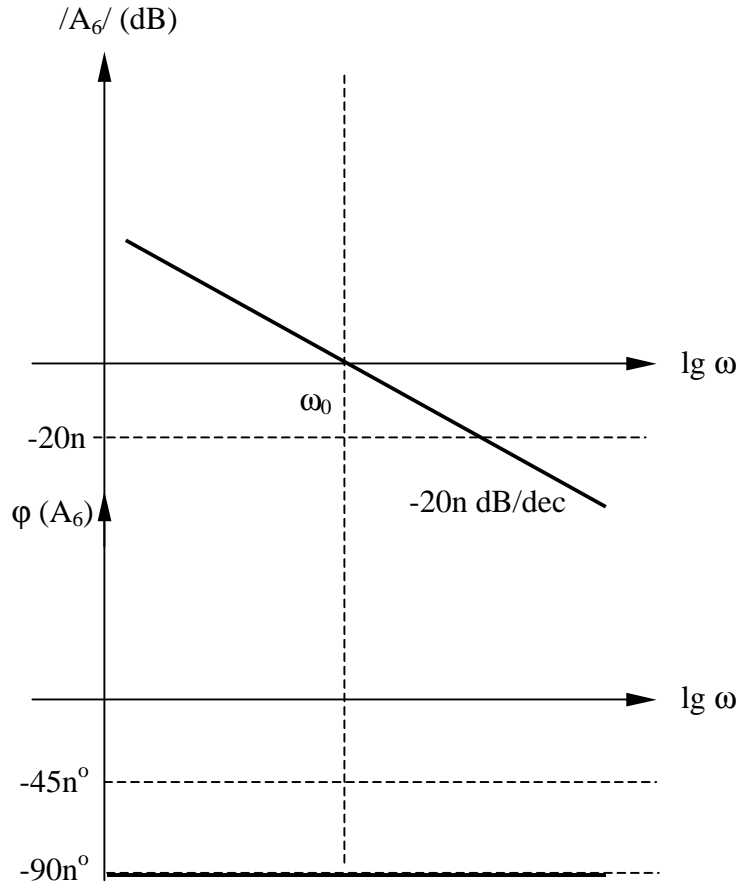


$$A_6 = \frac{I}{\left(j \frac{\omega}{\omega_0}\right)^n}$$

$$|A_6| = -20 \times n \lg \left( \frac{\omega}{\omega_0} \right)$$

$$\varphi(A_6) = -n \times 90^\circ$$

## A multiple zero

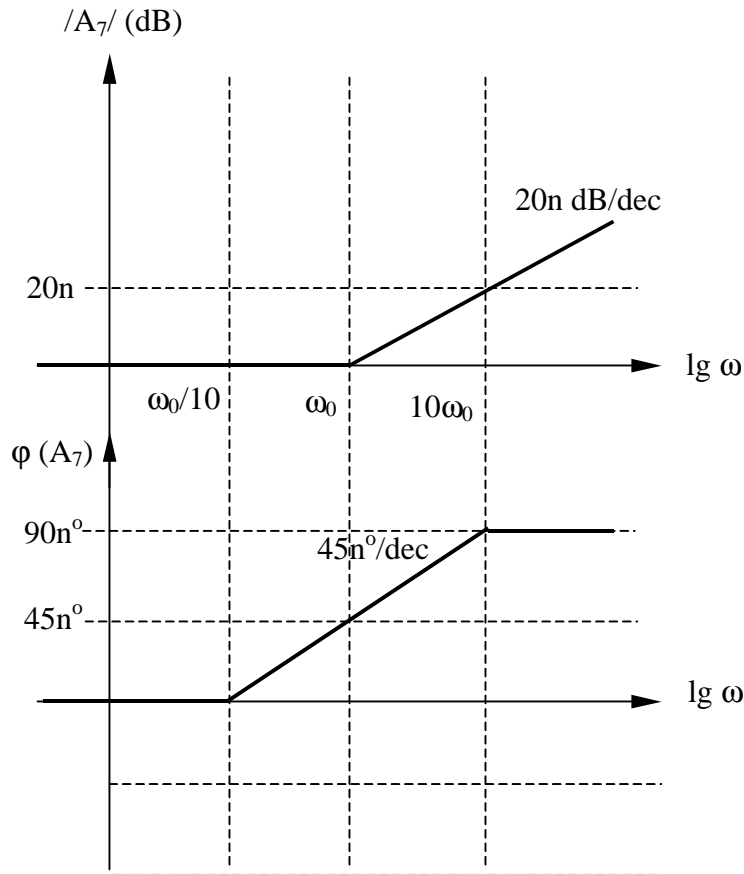

$$A_7 = \left( 1 + j \frac{\omega}{\omega_0} \right)^n$$


$$|A_7| = -20 \times n \lg \left[ \sqrt{1 + \left( \frac{\omega}{\omega_0} \right)^2} \right]$$

$$\omega \ll \omega_0 \Rightarrow |A_7| \rightarrow 0$$

$$\omega \gg \omega_0 \Rightarrow |A_7| \rightarrow -20 \times n \lg \left( \frac{\omega}{\omega_0} \right)$$

$$\varphi(A_7) = -n \times \text{arctg} \left( \frac{\omega}{\omega_0} \right)$$

# A multiple pole

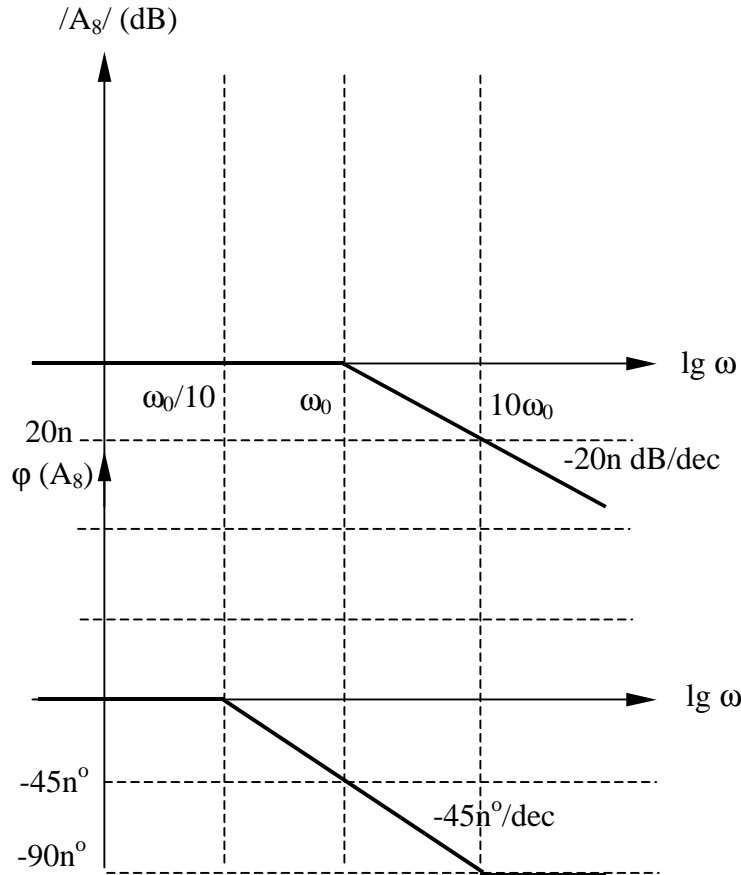

$$A_8 = \frac{1}{\left(1 + j \frac{\omega}{\omega_0}\right)^n}$$

$$|A_8| = -20 \times n \lg \left[ \sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2} \right]$$


$$\omega \ll \omega_0 \Rightarrow |A_8| \rightarrow 0$$

$$\omega \gg \omega_0 \Rightarrow |A_8| \rightarrow -20 \times n \lg \left( \frac{\omega}{\omega_0} \right)$$

$$\varphi(A_8) = -n \times \arctg \left( \frac{\omega}{\omega_0} \right)$$

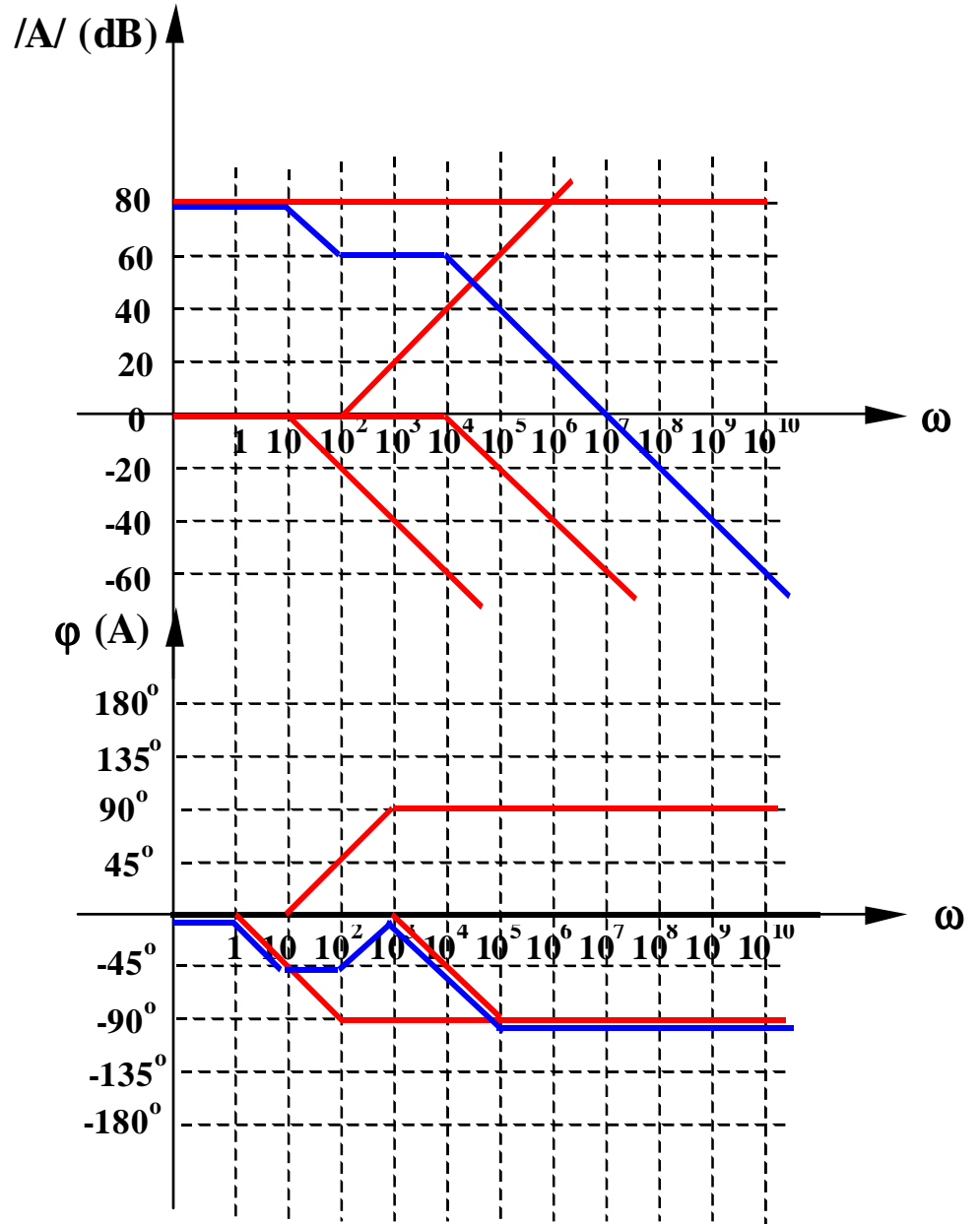
# Example 1

$$A(j\omega) = 10^4 \frac{1 + j \frac{\omega}{10^2}}{\left(1 + j \frac{\omega}{10}\right) \left(1 + j \frac{\omega}{10^4}\right)}$$



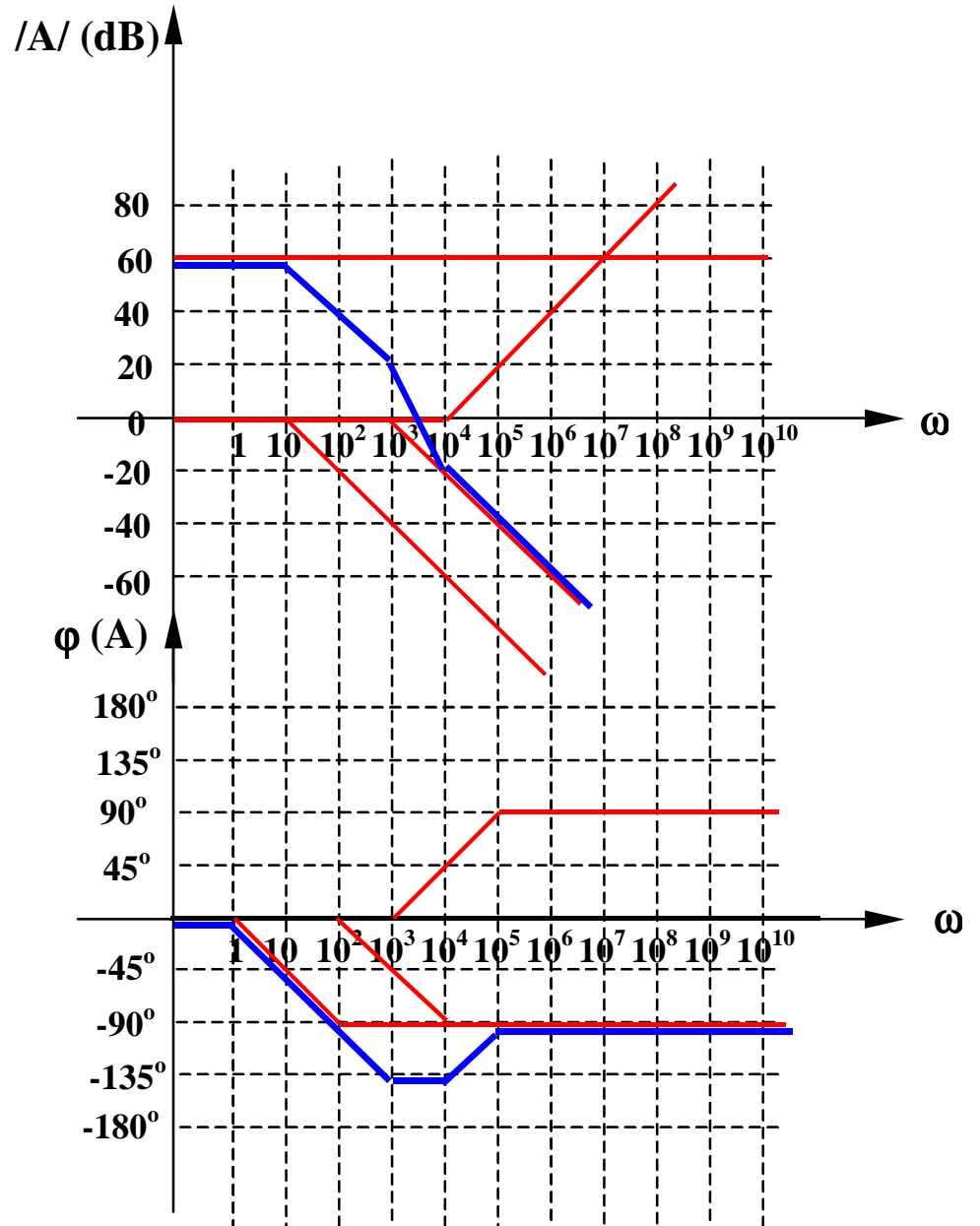
# Example 2

$$A(j\omega) = 10^3 \frac{1 + j \frac{\omega}{10^4}}{\left(1 + j \frac{\omega}{10}\right) \left(1 + j \frac{\omega}{10^3}\right)}$$






## 6.1.3. Miller theorem

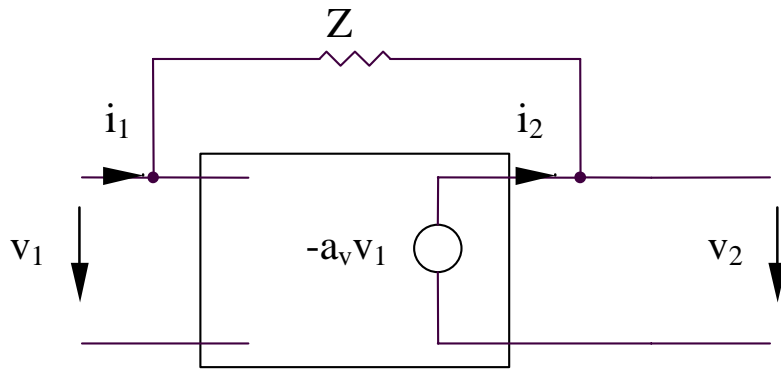

(a)

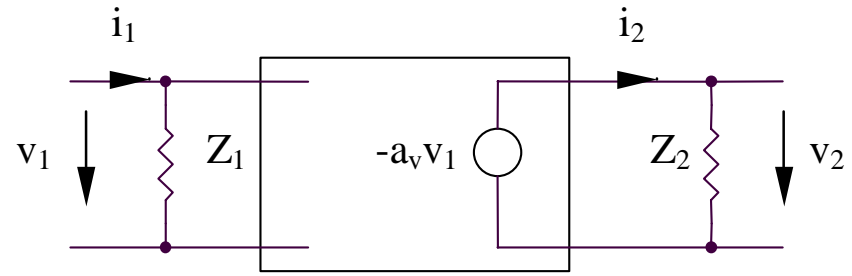

(b)

$$i_1 = \frac{v_1 - v_2}{Z} = \frac{v_1 + a_v v_1}{Z} = \frac{(1 + a_v)v_1}{Z}$$

$$i_2 = \frac{v_2 - v_1}{Z} = -\frac{(1 + a_v)v_1}{Z}$$

$$i_1 = \frac{v_1}{Z_1}$$

$$i_2 = \frac{v_2}{Z_2} = -\frac{a_v v_1}{Z_2}$$


$$\Rightarrow Z_1 = \frac{Z}{1 + a_v} \ll Z; \quad Z_2 = Z \frac{a_v}{1 + a_v} \cong Z$$

### **6.1.3. Miller theorem**

## **6.2. Amplifiers with reaction**

## **6.2.1. The block diagram of the amplifier with reaction**
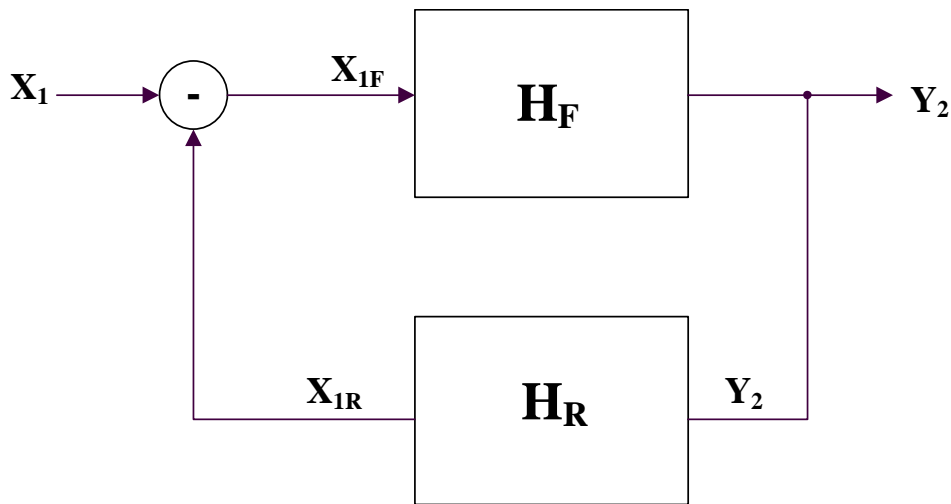
## 6.2.1. The block diagram of the amplifier with reaction



$$Y_2 = H_F X_{1F}$$

$$X_{1R} = H_R Y_2$$

$$X_{1F} = X_1 - X_{1R} = X_1 - H_F H_R X_{1F}$$

$X_1, Y_2$  are currents/voltages

$$\text{The global gain: } H = \frac{Y_2}{X_1} = \frac{H_F}{1 + H_R H_F}$$

## 6.2.2. Types of reaction

- Positive reaction:  $|H| > |H_F|$        $|1 + H_F H_R| < 1$

- Negative reaction:  $|H| < |H_F|$        $|1 + H_F H_R| > 1$

Particular case: strong negative reaction

Defining loop transmission:  $T = \frac{X_{1R}}{X_{1F}} = H_F H_R \gg 1$  ( $|H| \ll |H_F|$ )

it results  $H|_{T \gg 1} = \frac{H_F}{H_F H_R} = \frac{1}{H_R}$  - independent on amplifier

**Conclusion:** *for strong negative reaction, the gain with reaction is function only on reaction*

## **6.2.2. Types of reaction**

## **6.3. Reaction effects**



### **6.3.1. Amplifier de-sensitivity**

### 6.3.1. Amplifier de-sensitivity

$$\frac{dH}{dH_F} = \frac{d}{dH_F} \left( \frac{H_F}{1 + H_F H_R} \right) = \frac{1}{(1 + H_F H_R)^2}$$

$$\left| \frac{dH}{H} \right| = \frac{1}{|1 + H_R H_F|} \left| \frac{dH_F}{H_F} \right| = \frac{1}{|F|} \left| \frac{dH_F}{H_F} \right|$$

$$F = 1 + H_R H_F = 1 + T$$

(reaction factor)

### **6.3.2. Distortion reduction**

## **6.3.2. Distortion reduction**

*The reaction reduces the effect of distortions.*

### **6.3.3. The improving of frequency response**

### 6.3.3. The improving of frequency response

For  $\omega_{\min}$

Supposing that the direct amplifier is characterized by a first-order function:


$$H_F(j\omega) = H_{F0} \frac{j\omega}{\omega_{F\min} + j\omega}$$

and that we have a constant negative reaction  $H_{R0}$ ,  
it results:

$$H(j\omega) = \frac{H_F(j\omega)}{1 + H_F(j\omega)H_{R0}}$$

resulting:
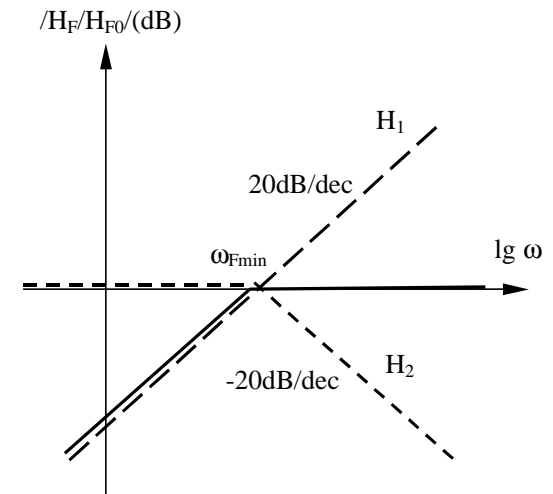
$$H(j\omega) = \frac{H_{F0} \frac{j\omega}{\omega_{F\min}}}{1 + \frac{j\omega}{\omega_{F\min}} + H_{F0}H_{R0} \frac{j\omega}{\omega_{F\min}}}$$



equivalent with:

$$H(j\omega) = \frac{H_{F0}}{1 + H_{F0}H_{R0}} \frac{\frac{j\omega}{\omega_{F \min}} (1 + H_{F0}H_{R0})}{1 + \frac{j\omega}{\omega_{F \min}} (1 + H_{F0}H_{R0})}$$

It is possible to find the following form of  $H(j\omega)$ :


$$H(j\omega) = H_0 \frac{\frac{j\omega}{\omega_{\min}}}{1 + \frac{j\omega}{\omega_{\min}}}$$

where:

$$H_0 = \frac{H_{F0}}{1 + H_{F0}H_{R0}}$$

$$\omega_{\min} = \frac{\omega_{F \min}}{1 + H_{F0}H_{R0}}$$

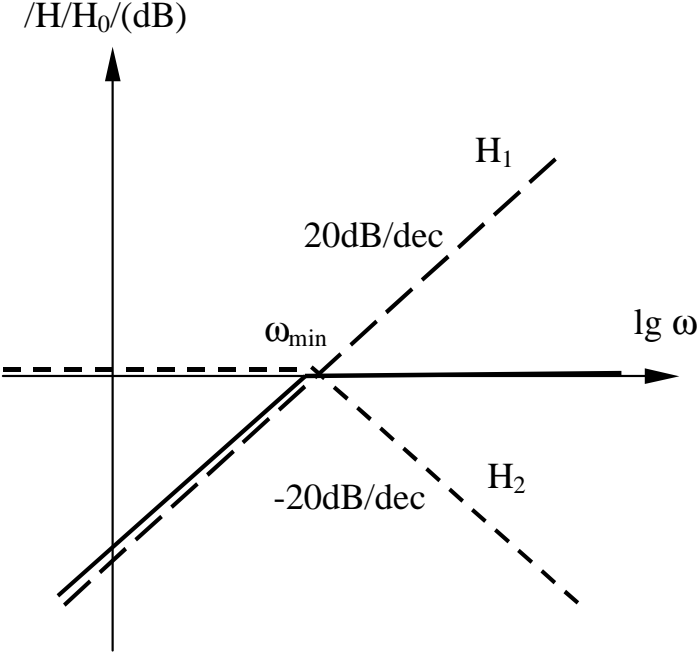**Conclusion:** *The amplifier bandwidth is increased with the same factor of the gain decreasing.*





### 6.3.3. The improving of frequency response

For  $\omega_{\max}$

Supposing that the direct amplifier is characterized by a first-order function:


$$H_F(j\omega) = \frac{H_{F0}}{1 + \frac{j\omega}{\omega_{F \max}}}$$

and that we have a constant negative reaction  $H_{R0}$ ,  
it results:

$$H(j\omega) = \frac{H_F(j\omega)}{1 + H_F(j\omega)H_{R0}}$$

resulting:
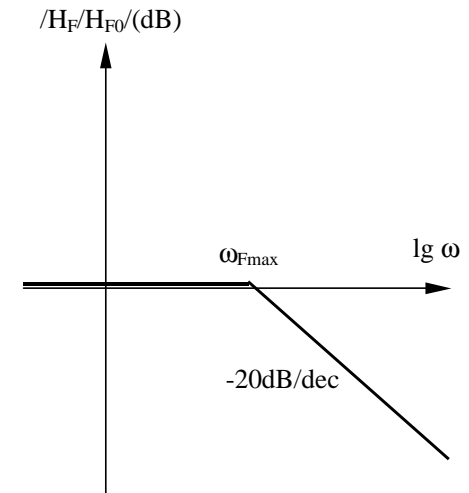
$$H(j\omega) = \frac{H_{F0}}{1 + H_{F0}H_{R0} + \frac{j\omega}{\omega_{F \max}}}$$



**equivalent with:**

$$H(j\omega) = \frac{H_{F0}}{1 + H_{F0}H_{R0}} \frac{H_{F0}}{1 + \frac{j\omega}{\omega_{F \max}(1 + H_{F0}H_{R0})}}$$

**It is possible to find the following form of  $H(j\omega)$ :**


$$H(j\omega) = H_0 \frac{1}{1 + \frac{j\omega}{\omega_{\max}}}$$

**where:**

$$H_0 = \frac{H_{F0}}{1 + H_{F0}H_{R0}}$$


$$\omega_{\max} = \omega_{F \max}(1 + H_{F0}H_{R0})$$

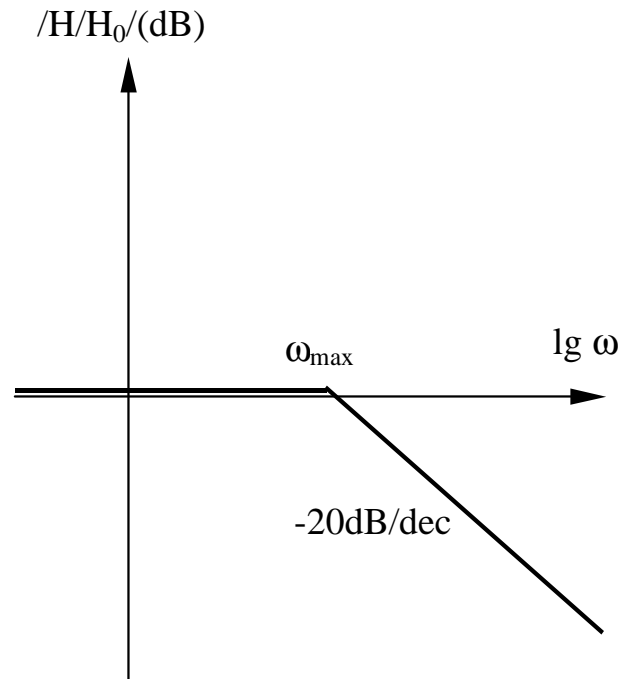**Conclusion:** *The amplifier bandwidth is increased with the same factor of the gain decreasing.*



### 6.3.3. The improving of frequency response

**Conclusion:**

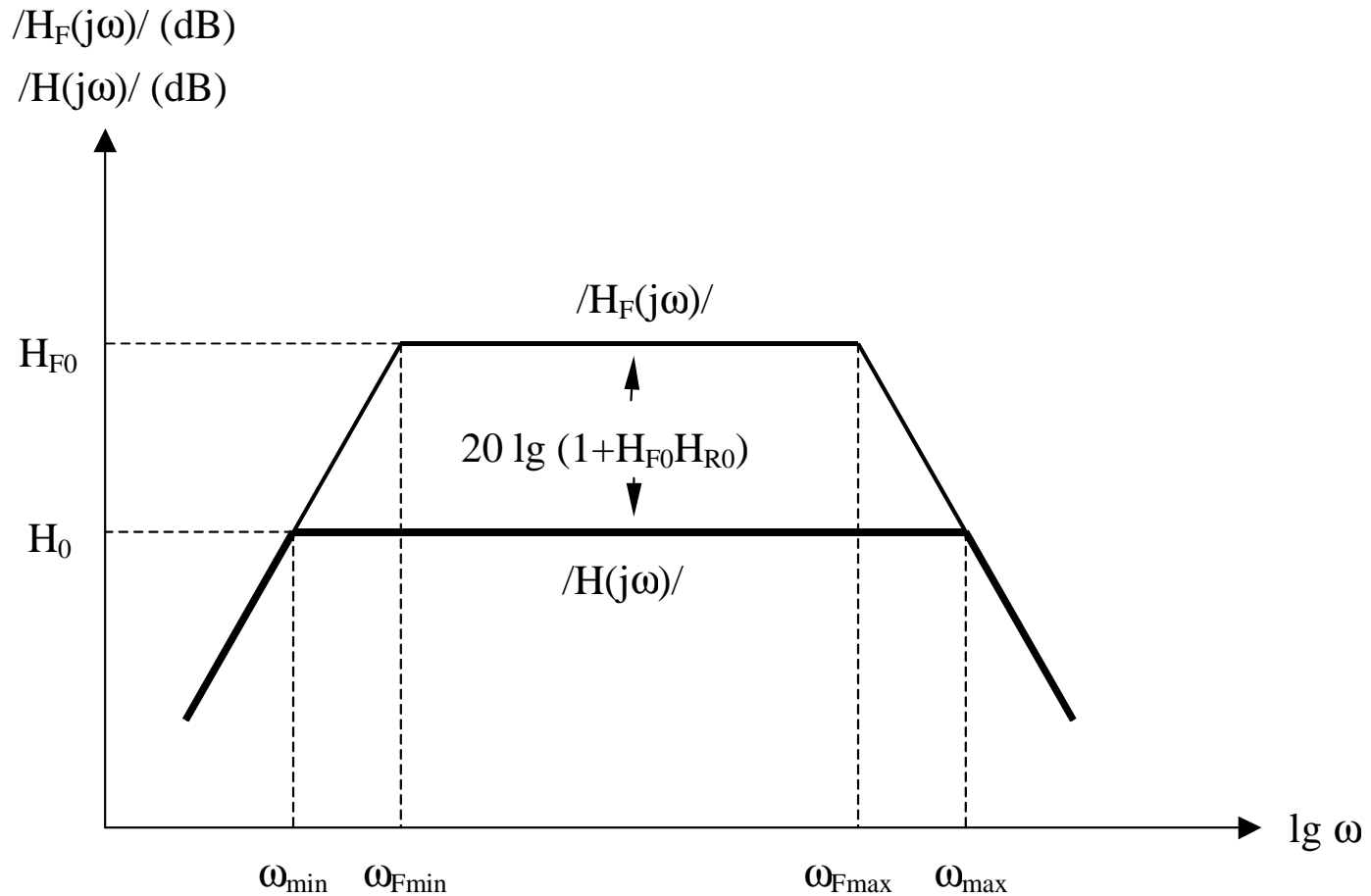

### **6.3.4. The impact on input/output resistances**

### 6.3.4. The impact on input/output resistances

**The reaction changes input/output resistances in such a way that the amplifier with reaction simulates better an ideal amplifier.**

$$R_i' = R_i (1 + T) \quad \text{for series reactions}$$

$$R_i' = R_i (1 + T)^{-1} \quad \text{for parallel reactions}$$

$$R_o' = R_o (1 + T) \quad \text{for series reactions}$$

$$R_o' = R_o (1 + T)^{-1} \quad \text{for parallel reactions}$$

## **6.4. Circuits stability**

## **6.4.1. Algorithm for evaluating the stability of a circuit**




## 6.4.1. Algorithm for evaluating the stability of a circuit

1. Annulate the input voltage
2. Split the reaction loop in an arbitrary point
3. Apply a test voltage in this point,  $V_{\text{test}}$
4. Calculate the “return” voltage in the same point,  $V_{\text{tr}}$
5. Compute the Return Ratio  $T = V_{\text{tr}}/V_{\text{test}}$
6. Represent the Bode diagrams for  $T$
7. Represent an horizontal line at  $-180^\circ$ 
  - A. If the horizontal does not intersect the phase graphic, the circuit is stable
  - B. If the horizontal intersects the phase graphic in a point A, from A represent a vertical axis which intersects the module diagram in point B
    - a. if  $\angle T|_B > 0$ , the circuit is not stable
    - b. if  $\angle T|_B = 0$ , the circuit at the stability limit
    - c. if  $\angle T|_B < 0$ , the circuit is stable. In this case it is possible to determine the phase margin: mark with C the point in which  $\angle T = 0$ , represent a vertical axis from this point, which will intersect the phase diagram in point D. The phase margin is  $\Delta\varphi = 180^\circ + \varphi(D)$



## **6.4.2. Example 1**
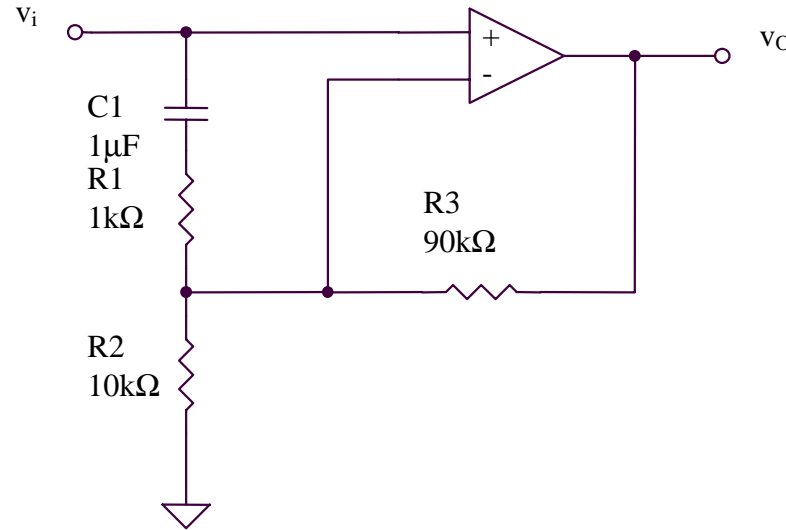
## 6.4.2. Example 1

Evaluate the stability of the following circuit



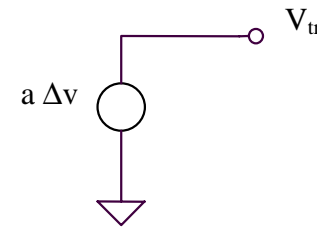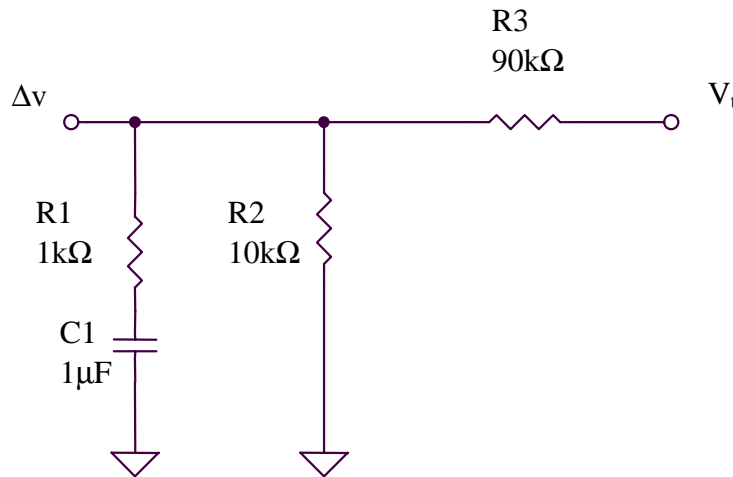
$$a(j\omega) = \frac{10^5}{1 + j\frac{\omega}{10}}$$



$$T = \frac{V_{tr}}{V_t} = \frac{a\Delta v}{V_t} = a \frac{R_2 // (R_1 + X_{C1})}{R_2 // (R_1 + X_{C1}) + R_3}$$

$$T = a \frac{\frac{R_2(1 + j\omega C_1 R_1)}{1 + j\omega C_1(R_1 + R_2)}}{\frac{R_2(1 + j\omega C_1 R_1)}{1 + j\omega C_1(R_1 + R_2)} + R_3} = a \frac{R_2}{R_2 + R_3} \frac{1 + j\omega C_1 R_1}{1 + j\omega C_1 [R_1 + (R_2 // R_3)]}$$
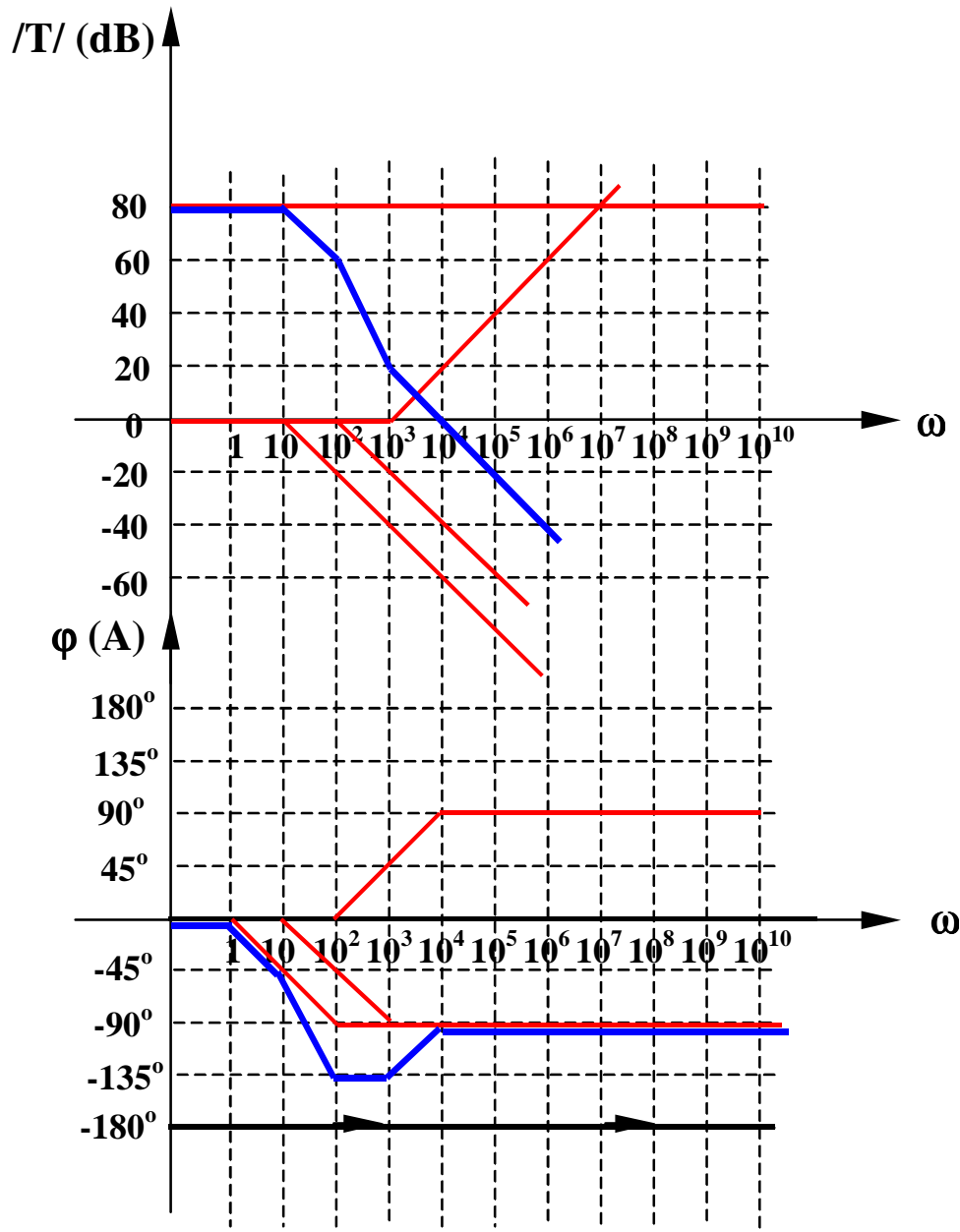
$$T = 10^4 \frac{1 + j \frac{\omega}{10^3}}{\left(1 + j \frac{\omega}{10}\right) \left(1 + j \frac{\omega}{10^2}\right)}$$




**The horizontal line does not intersect the phase diagram, so the circuit is stable.**



### **6.4.3. Example 2**
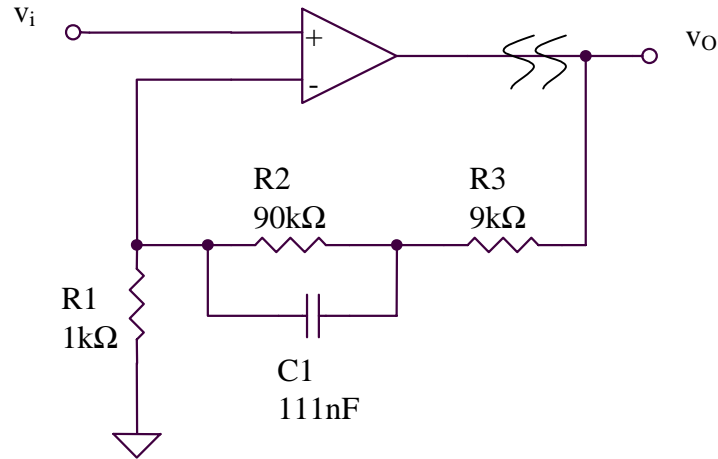
### 6.4.3. Example 2

Evaluate the stability of the following circuit


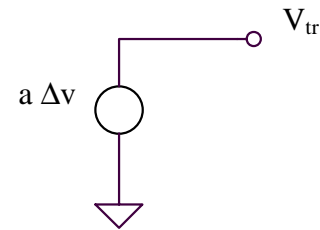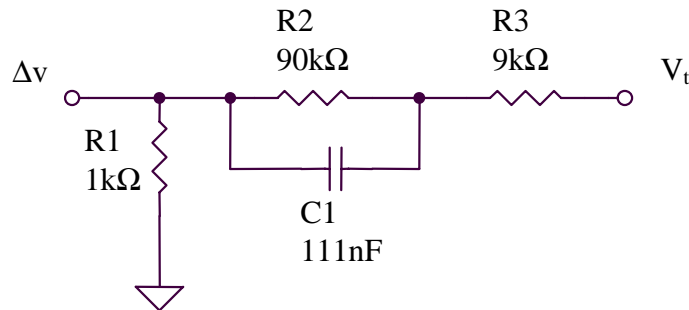
$$a(j\omega) = \frac{10^5}{1 + j\frac{\omega}{10}}$$




$$T = \frac{V_{tr}}{V_t} = \frac{a\Delta v}{V_t} = a \frac{R_1}{R_1 + R_3 + R_2 // X_{C1}}$$

$$T = a \frac{R_1}{R_1 + R_3 + \frac{R_2}{1 + j\omega C_1 R_2}} = a \frac{R_1}{R_1 + R_2 + R_3} \frac{1 + j\omega C_1 R_2}{1 + j\omega C_1 [R_2 // (R_1 + R_3)]}$$
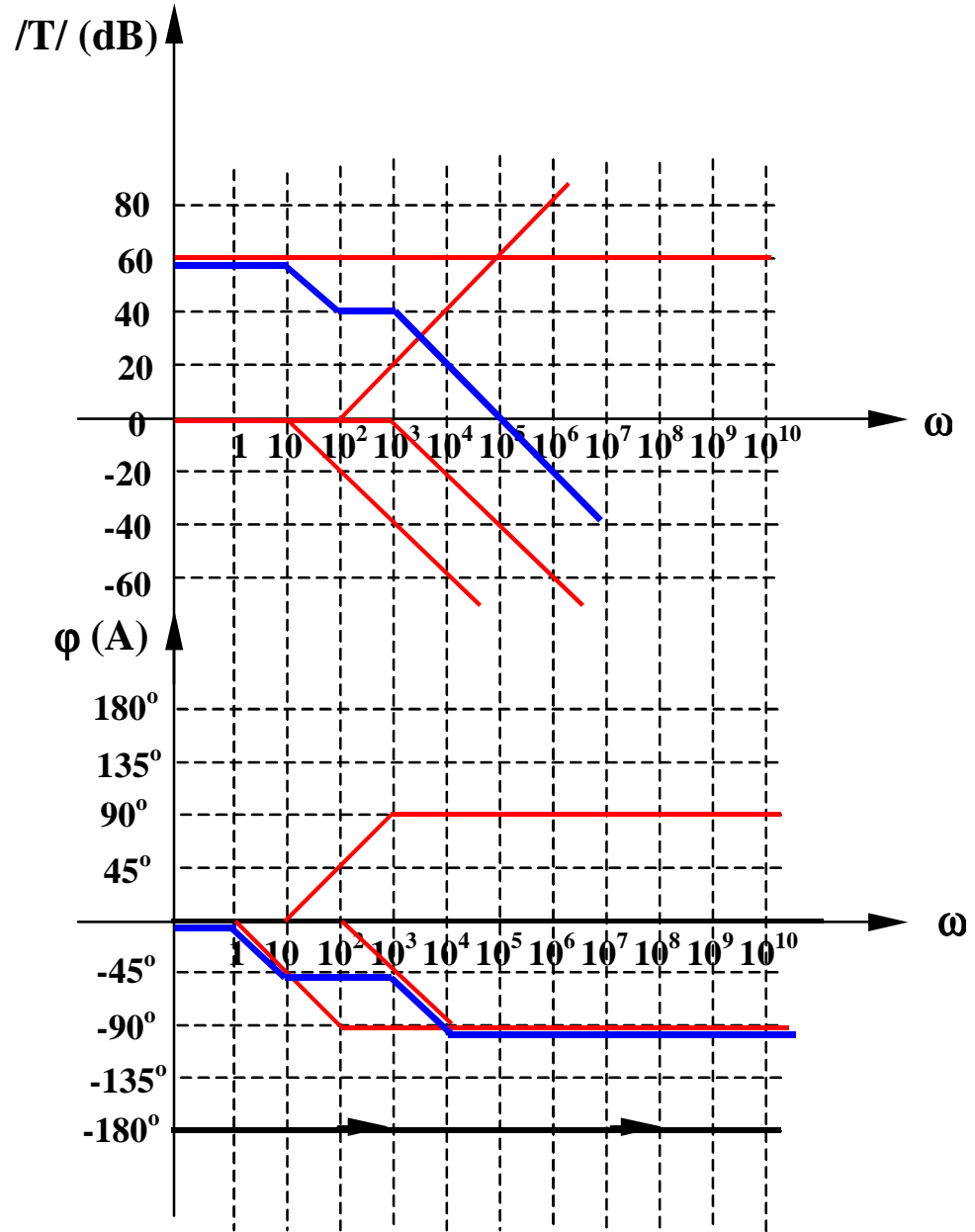
$$T = 10^3 \frac{1 + j \frac{\omega}{10^2}}{\left(1 + j \frac{\omega}{10}\right) \left(1 + j \frac{\omega}{10^3}\right)}$$






**The horizontal line does not intersect the phase diagram, so the circuit is stable.**



### **6.4.4. Exemple 3**
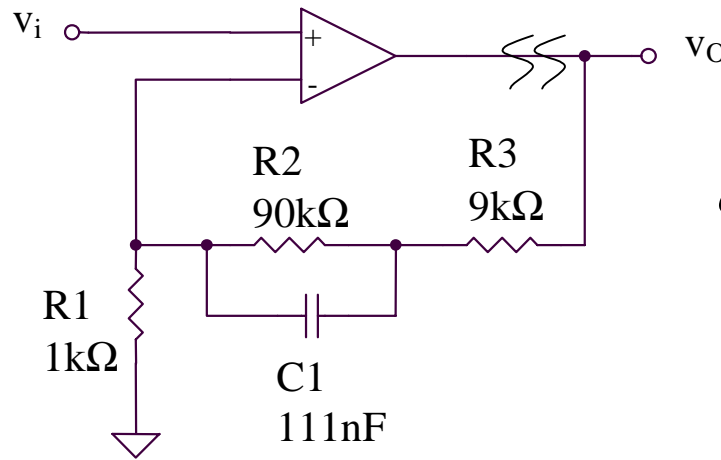
### 6.4.4. Exemple 3

Evaluate the stability of the following circuit



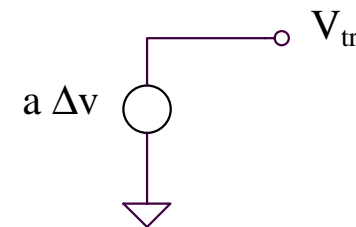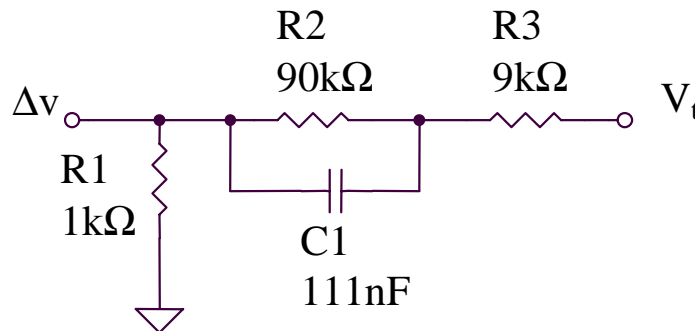
$$a(j\omega) = \frac{10^5}{\left(1 + j\frac{\omega}{10}\right)\left(1 + j\frac{\omega}{10^5}\right)^2}$$



$$T = \frac{V_{tr}}{V_t} = \frac{a\Delta v}{V_t} = a \frac{R_1}{R_1 + R_3 + R_2 // X_{C1}}$$

$$T = a \frac{R_1}{R_1 + R_3 + \frac{R_2}{1 + j\omega C_1 R_2}} = a \frac{R_1}{R_1 + R_2 + R_3} \frac{1 + j\omega C_1 R_2}{1 + j\omega C_1 [R_2 // (R_1 + R_3)]}$$
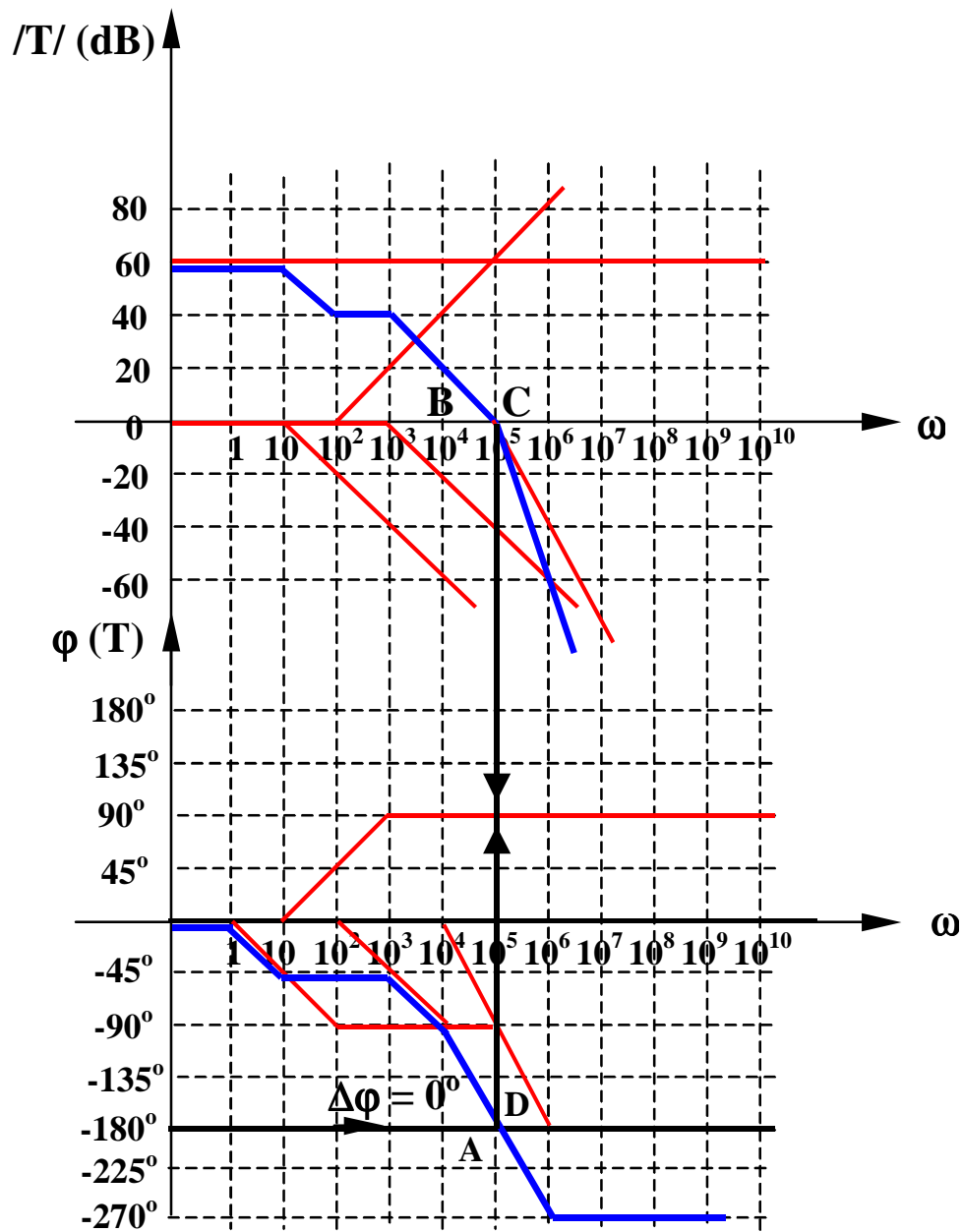
$$T = 10^3 \frac{1 + j\frac{\omega}{10^2}}{\left(1 + j\frac{\omega}{10}\right)\left(1 + j\frac{\omega}{10^3}\right)\left(1 + j\frac{\omega}{10^5}\right)^2}$$



The horizontal line at  $-180^\circ$  intersects the phase diagram in A point,  $|T_B| = 0$ , so the circuit is at the stability limit ( $\Delta\phi = 0$ ).